

Step and Impulse Response of an RLC Bandpass Filter

Prelab 5

Spring 2024

1 Purpose

Use Laplace transforms to find the time-domain step- and impulse-response of an RLC bandpass filter.

2 Deliverables Overview

Typed solutions for **Task 1** and **Task 2**. *Note: Be sure to show all work. All math must be solved symbolically in terms of R , L , C .*

3 Tasks

Consider the RLC circuit in figure 1.

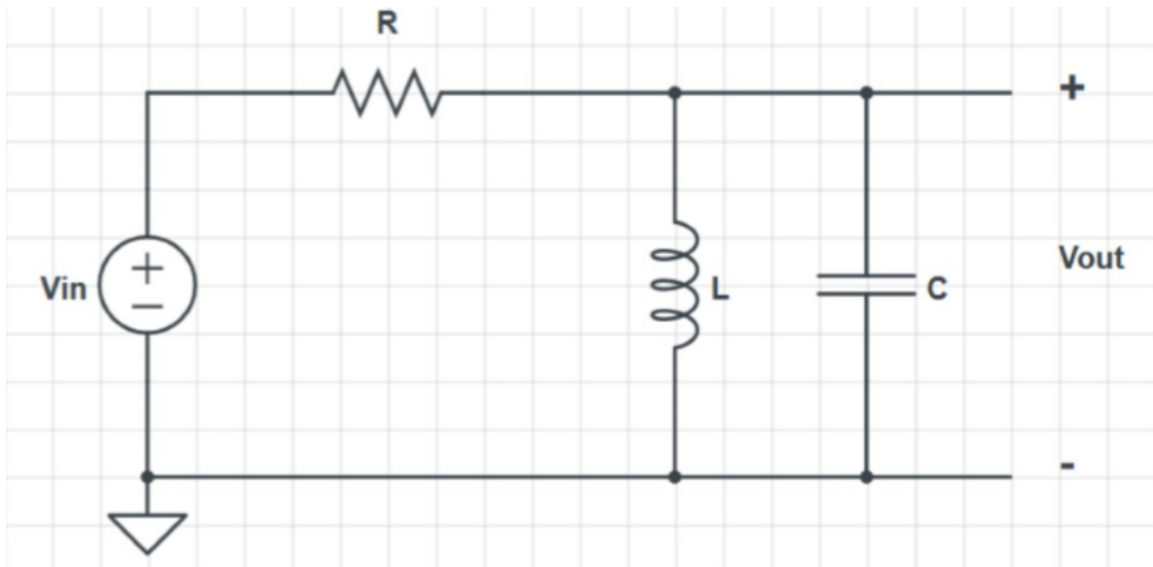


Figure 1: $R = 1\text{k}\Omega$, $L = 27\text{ mH}$, $C = 100\text{ nF}$

1. Find the transfer function $H(s) = \frac{V_{out}(s)}{V_{in}(s)}$.
2. Find the impulse response $h(t)$.