

# Frequency Response

Prelab 10

Spring 2024

## 1 Purpose

Find the analytical expression for the magnitude and phase of a transfer function.

## 2 Deliverables Overview

- Typed and properly formatted derivation for both the magnitude and phase of the transfer function. *Note: All steps must be shown.*

## 3 Part 1

### 3.1 Tasks

Consider the RLC circuit in Figure 1.

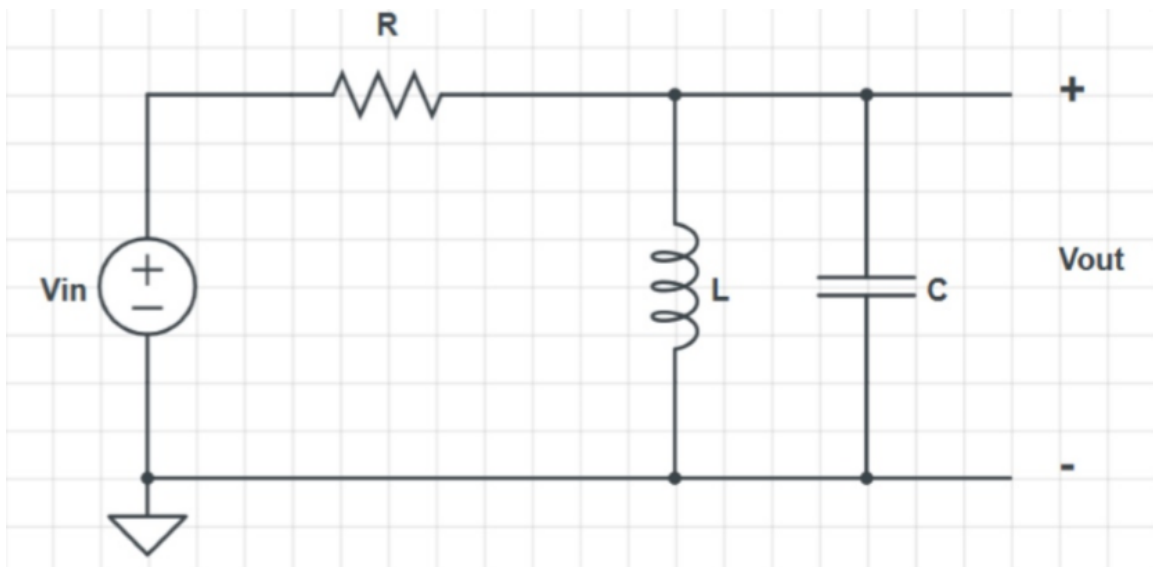


Figure 1:  $R = 1 \text{ k}\Omega$ ,  $L = 27 \text{ mH}$ ,  $C = 100 \text{ nF}$

Which has the transfer function,

$$H(s) = \frac{\frac{1}{RC}s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}.$$

1. By hand, find the magnitude  $|H(j\omega)|$  and the phase  $\angle H(j\omega)$  for the RLC transfer function  $H(s)$ . Do not use your calculator or Python in this step, show all your work.